 


Modeling FSMs in SV

Modeling FSMs





■ TABLE 5-1
State Table for Circuit of Figure 5-15

Present State		Input	Next State		Output
A	B	X	A	B	Y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

- We need to describe the following objects.
 - States: enumerated types
 - Next state function (State transition table): case statement
 - Output function: case statement
 - Transfer from the Current State to Next State: always statement

Modeling Decisions: Moore FSM

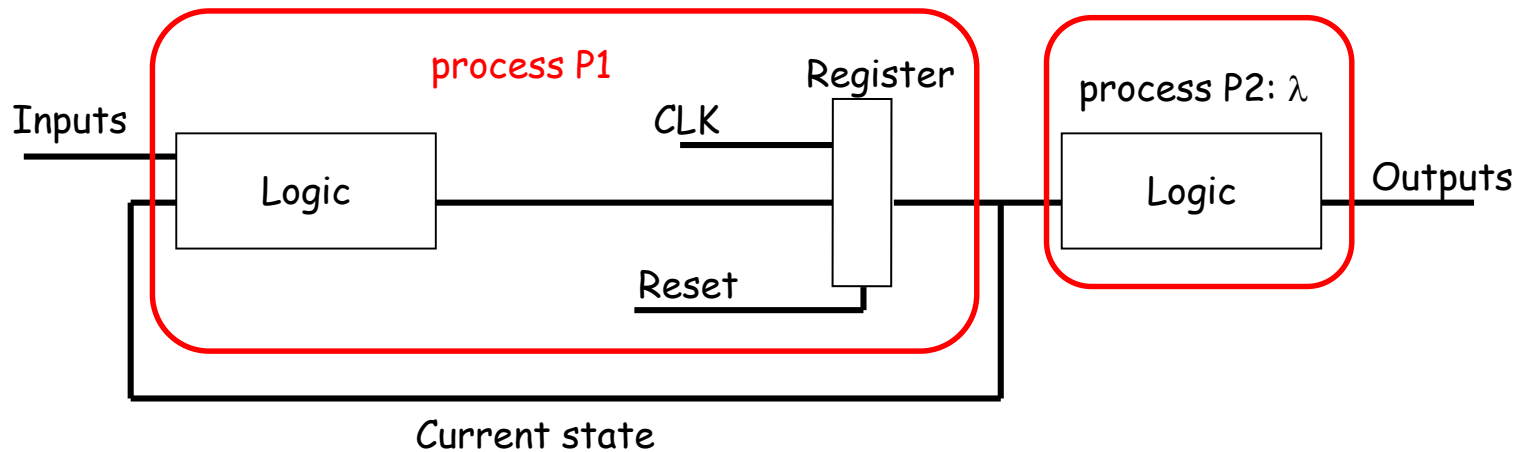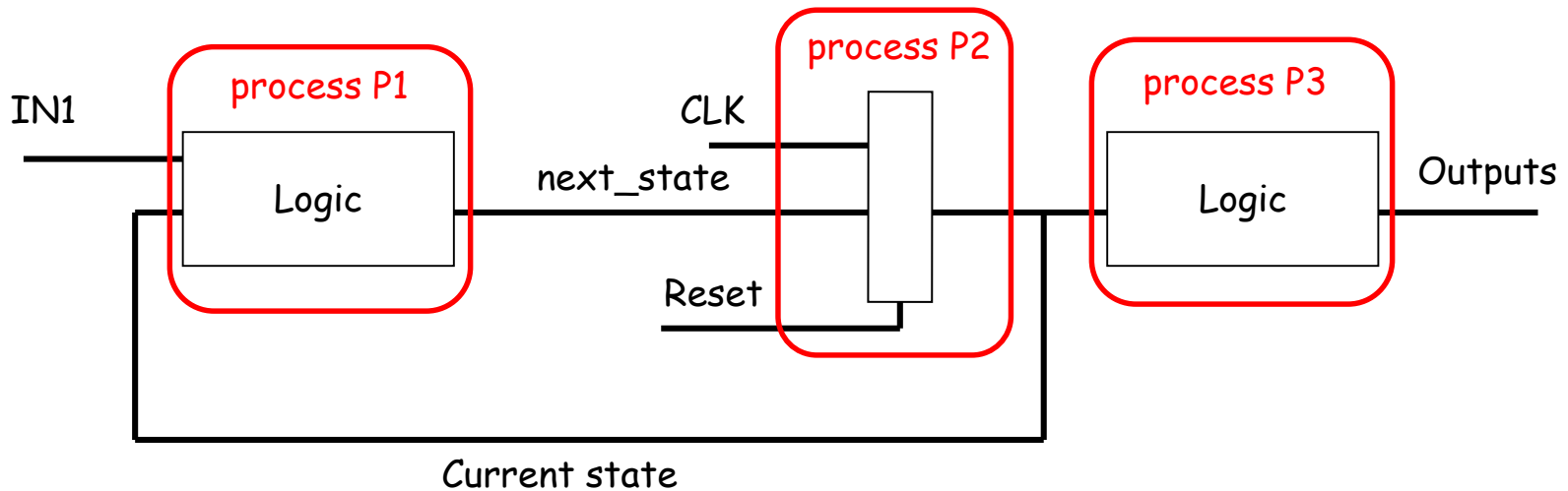

Modeling States

- The state of the system must be held in an internal register.
- In SystemVerilog, the state can be represented by an *enumerated type*.
- The possible values of this type are the state names and
 - the name of the variable is given after the list of values,
 - e.g. **enum** {s0, s1, ...} state;

Moore FSM

```
module divideby3FSM(input logic clk,
                    input logic reset,
                    output logic y);
    typedef enum logic [1:0] {S0, S1, S2} statetype;
    statetype [1:0] state, nextstate;
    // state register
    always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
        else state <= nextstate;
    // next state logic
    always_comb
    case (state)
        S0: nextstate = S1;
        S1: nextstate = S2;
        S2: nextstate = S0;
        default: nextstate = S0;
    endcase
    // output logic
    assign y = (state == S0);
endmodule
```

- `typedef` defines `statetype` to be a two-bit logic value with S0, S1, or S2.
- `state` and `nextstate` are `statetype` signals.
- The enumerated `encodings default` to numerical order: S0 = 00, S1 = 01, and S2 = 10.
- The encodings can be explicitly set by the user; however, the synthesis tool views them as suggestions, not requirements.
- For example, 3-bit one-hot encoding:
`typedef enum logic [2:0] {S0 = 3'b001, S1 = 3'b010, S2 = 3'b100} statetype;`

Moore FSM

```
module patternMoore(input logic clk,
                    input logic reset,
                    input logic a,
                    output logic y);
typedef enum logic [1:0] {S0, S1, S2}
statetype;
statetype state, nextstate;
// state register
always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else state <= nextstate;
// next state logic
always_comb
    case (state)
        S0: if (a) nextstate = S0;
            else nextstate = S1;
        S1: if (a) nextstate = S2;
            else nextstate = S1;
        S2: if (a) nextstate = S0;
            else nextstate = S1;
        default: nextstate = S0;
    endcase
// output logic
assign y = (state == S2);
endmodule
```

- Nonblocking assignments (<=) are used in the state register to describe sequential logic
- Blocking assignments (=) are used in the next state logic to describe combinational logic.

```

module patternMoore(input logic clk,
                    input logic reset,
                    input logic a,
                    output logic y);
typedef enum logic [1:0] {S0, S1, S2} statetype;
statetype state, nextstate;
// state register
always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else state <= nextstate;
// next state logic
always_comb
    case (state)
        S0: if (a) nextstate = S0;
            else nextstate = S1;
        S1: if (a) nextstate = S2;
            else nextstate = S1;
        S2: if (a) nextstate = S0;
            else nextstate = S1;
        default: nextstate = S0;
    endcase
// output logic
assign y = (state == S2);
endmodule

```

Moore

```

module patternMealy(input logic clk,
                    input logic reset,
                    input logic a,
                    output logic y);
typedef enum logic {S0, S1} statetype;
statetype state, nextstate;
// state register
always_ff @(posedge clk, posedge reset)
    if (reset) state <= S0;
    else state <= nextstate;
// next state logic
always_comb
    case (state)
        S0: if (a) nextstate = S0;
            else nextstate = S1;
        S1: if (a) nextstate = S0;
            else nextstate = S1;
        default: nextstate = S0;
    endcase
// output logic
assign y = (a & state == S1);
endmodule

```

Mealy

Enumerated Types + Unique Case

```
module traffic_light (output logic green_light,
                      yellow_light,
                      red_light,
                      input      sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input      clock, resetN);

enum {RED, GREEN, YELLOW} State, Next; // using enum defaults

always_ff @(posedge clock, negedge resetN)
  if (!resetN) State <= RED; // reset to red light
  else        State <= Next;

always_comb begin: set_next_state
  Next = State; // the default for each branch below
  unique case (State)
    RED:   if (sensor)           Next = GREEN;
    GREEN: if (green_downcnt == 0) Next = YELLOW;
    YELLOW: if (yellow_downcnt == 0) Next = RED;
  endcase
end: set_next_state

always_comb begin: set_outputs
  {green_light, yellow_light, red_light} = 3'b000;
  unique case (State)
    RED:   red_light   = 1'b1;
    GREEN: green_light = 1'b1;
    YELLOW: yellow_light = 1'b1;
  endcase
end: set_outputs
endmodule
```

- By using enumerated types, the only possible values of the State and Next variables are the ones listed in their enumerated type lists.
- The unique modifier to the case statements in the state machine logic helps confirm that the case statements cover all possible values of the State and Next variables

Default (int) -> logic

- It uses the **default** enum base type of **int**, and the default values for each value label (0, 1 and 2, respectively).
- These defaults might not accurately reflect hardware behavior in simulation.
 - The **int** type is a 32-bit 2-state type.
 - The real hardware only needs a 2- or 3-bit vector, depending on state coding.
- The gate-level model of the implementation will have 4-state semantics.
- **Solution: Use logic as Based Type**

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input
                    clock, resetN);

enum {RED, GREEN, YELLOW} State, Next; // using enum defaults

always_ff @(posedge clock, negedge resetN)
    if (!resetN) State <= RED; // reset to red light
    else          State <= Next;

always_comb begin: set_next_state
    Next = State; // the default for each branch below
    unique case (State)
        RED:    if (sensor)          Next = GREEN;
        GREEN:  if (green_downcnt == 0) Next = YELLOW;
        YELLOW: if (yellow_downcnt == 0) Next = RED;
    endcase
end: set_next_state

always_comb begin: set_outputs
    {green_light, yellow_light, red_light} = 3'b000;
    unique case (State)
        RED:    red_light    = 1'b1;
        GREEN:  green_light  = 1'b1;
        YELLOW: yellow_light = 1'b1;
    endcase
end: set_outputs
endmodule
```

Explicit Enumeration Label Values

- Since the values for the enumerated labels were not explicitly specified, synthesis compilers might optimize the gate-level implementation to different values for each state.
- This makes it more difficult to compare the pre- and post-synthesis model functionality, or to specify assertions that work with both the pre- and post-synthesis models.
- **Solution: Explicit Enumeration Label Values**

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input      sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input      clock, resetN);

    enum {RED, GREEN, YELLOW} State, Next; // using enum defaults

    always_ff @(posedge clock, negedge resetN)
        if (!resetN) State <= RED; // reset to red light
        else          State <= Next;

    always_comb begin: set_next_state
        Next = State; // the default for each branch below
        unique case (State)
            RED:    if (sensor)          Next = GREEN;
            GREEN:  if (green_downcnt == 0) Next = YELLOW;
            YELLOW: if (yellow_downcnt == 0) Next = RED;
        endcase
    end: set_next_state

    always_comb begin: set_outputs
        {green_light, yellow_light, red_light} = 3'b000;
        unique case (State)
            RED:    red_light  = 1'b1;
            GREEN:  green_light = 1'b1;
            YELLOW: yellow_light = 1'b1;
        endcase
    end: set_outputs
endmodule
```

Explicit Encoding => Consistency

- The enumerated label values that represent the state sequencing are **explicitly** specified in the RTL model.
- Synthesis compilers will retain these values in the gate-level implementation.
- This helps in comparing pre- and post-synthesis model functionality.
- It also makes it easier to specify verification assertions that work with both the pre- and post-synthesis models.

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input    sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input    clock, resetN);

enum logic [2:0] {RED    = 3'b001, // explicit enum definition
                 GREEN   = 3'b010,
                 YELLOW  = 3'b100} State, Next;

always_ff @(posedge clock, negedge resetN)
    if (!resetN) State <= RED; // reset to red light
    else          State <= Next;

always_comb begin: set_next_state
    Next = State; // the default for each branch below
    unique case (State)
        RED:    if (sensor)          Next = GREEN;
        GREEN:  if (green_downcnt == 0) Next = YELLOW;
        YELLOW: if (yellow_downcnt == 0) Next = RED;
    endcase
end: set_next_state

always_comb begin: set_outputs
    {green_light, yellow_light, red_light} = 3'b000;
    unique case (State)
        RED:    red_light  = 1'b1;
        GREEN:  green_light = 1'b1;
        YELLOW: yellow_light = 1'b1;
    endcase
end: set_outputs
endmodule
```

Optimization in Synthesis

- Synthesis compiler may provide a way to override the explicit enumeration label values, in order to optimize the gate-level implementation;
- This type of optimization cancels many of the benefits of specifying explicit enumeration values.

Unique Case with One-Hot

- The use of the **unique** modifier to the case statement in the preceding example is important.
- Since a one-hot state machine **only has one bit** of the state register set at a time,
 - only one of the case selection items will match the literal value of 1 in the case expression.

Regular Case Statements with Enumerated Types

- The **typical** use of a case statement is to
 - specify a variable as the case expression, and then
 - list explicit values to be matched as the list of case selection items.

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input      sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input      clock, resetN);

    enum logic [2:0] {RED    = 3'b001, // explicit enum definition
                     GREEN  = 3'b010,
                     YELLOW = 3'b100} State, Next;

    always_ff @(posedge clock, negedge resetN)
        if (!resetN) State <= RED; // reset to red light
        else          State <= Next;

    always_comb begin: set_next_state
        Next = State; // the default for each branch below
        unique case (State)
            RED:    if (sensor)          Next = GREEN;
            GREEN:  if (green_downcnt == 0) Next = YELLOW;
            YELLOW: if (yellow_downcnt == 0) Next = RED;
        endcase
    end: set_next_state

    always_comb begin: set_outputs
        {green_light, yellow_light, red_light} = 3'b000;
        unique case (State)
            RED:    red_light  = 1'b1;
            GREEN:  green_light = 1'b1;
            YELLOW: yellow_light = 1'b1;
        endcase
    end: set_outputs
endmodule
```

Regular Case: Vector Comparison

unique case (string) // vector

String :;

String :;

String :;

unique case (opcode)

3'b000: y = a + b;

3'b001: y = a - b;


3'b010: y = a * b;

3'b100: y = a / b;

endcase

Reversed Case: Single Bit Comparison
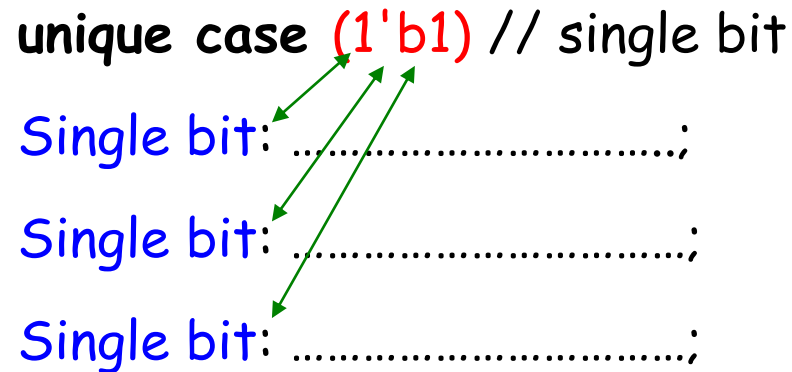
```
unique case (1'b1) // single bit
Single bit: .....;
Single bit: .....;
Single bit: .....;
```



Reversed Case Statements

```
enum {R_BIT = 0, // index of RED state in State register  
      G_BIT = 1, // index of GREEN state in State register  
      Y_BIT = 2} state_bit;  
enum logic [2:0] { RED = 3'b001<<R_BIT,  
                  GREEN = 3'b001<<G_BIT,  
                  YELLOW = 3'b001<<Y_BIT} State, Next;
```

```
RED      =001  
GREEN    =010  
YELLOW   =100
```

```
R_BIT = 0,  
G_BIT = 1,  
Y_BIT = 2
```

Reversed Case Statements

State is a 3-bit vector

State=(State[2], State[1], State[0])

RED =001

GREEN =010

YELLOW =100

R_BIT = 0,

G_BIT = 1,

Y_BIT = 2

1) State=001

unique case (1'b1)

State[0] = 1 :

State[1] = 0 :

State[2] = 0 :

2) State=010

unique case (1'b1)

State[0] = 0 :

State[1] = 1 :

State[2] = 0 :

3) State=100

unique case (1'b1)

State[0] = 0 :

State[1] = 0 :

State[2] = 1 :

Reversed Case Statements

- It has an effective hardware implementation.
- It can be used only for One-hot coding modeling.

```
unique case (1'b1) // reversed case statement
State[R_BIT]: if (sensor) Next = GREEN;
State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
```

Reversed Case Statements with Enumerated Types

```
module traffic_light ( output logic green_light,
                      yellow_light,
                      red_light,
                      input sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input clock, resetN);
enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;
// shift a 1 to the bit that represents each state
enum logic [2:0] { RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;
always_ff @(posedge clock, negedge resetN)
if (!resetN) State <= RED; // reset to red light
else State <= Next;
always_comb begin: set_next_state
Next = State; // the default for each branch below
```

```
unique case (1'b1) // reversed case statement
State[R_BIT]: if (sensor) Next = GREEN;
State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
endcase
end: set_next_state

always_comb begin: set_outputs
{red_light, green_light, yellow_light} = 3'b000;
unique case (1'b1) // reversed case statement
State[R_BIT]: red_light = 1'b1;
State[G_BIT]: green_light = 1'b1;
State[Y_BIT]: yellow_light = 1'b1;
endcase
end: set_outputs
endmodule
```

Reversed Case Statements

```
enum {R_BIT = 0, // index of RED state in State register  
      G_BIT = 1, // index of GREEN state in State register  
      Y_BIT = 2} state_bit;  
enum logic [2:0] { RED = 3'b001<<R_BIT,  
                  GREEN = 3'b001<<G_BIT,  
                  YELLOW = 3'b001<<Y_BIT} State, Next;
```

Logic Label	Label Internal Values
RED	=001
GREEN	=010
YELLOW	=100

<< shift operation

- `a = 5'b10100;`
- `b = a <<< 2; //b == 5'b10000`
- `c = a >>> 2; //c == 5'b11101, 'cause sign bit was `1``
- `d = a << 2; //d == 5'b10000`
- `e = a >> 2; //e == 5'b00101`

Reversed Case Statements with Enumerated Types

- An effective style for modeling one-hot state machines:
 - the case expression and the case selection items are reversed.
 - The case expression is specified as the literal value to be matched, which is a 1-bit value of 1.
 - The case selection items are each bit of the state variable.
- In some synthesis compilers, using the reversed case style for one-hot state machines might yield more optimized synthesis results than the standard style of case statements.

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input
                    clock, resetN);

enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;

// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

always_ff @(posedge clock, negedge resetN)
  if (!resetN) State <- RED; // reset to red light
  else
    State <- Next;

always_comb begin: set_next_state
  Next = State; // the default for each branch below
  unique case (1'b1) // reversed case statement
    State[R_BIT]: if (sensor) Next = GREEN;
    State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
    State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
  endcase
end: set_next_state

always_comb begin: set_outputs
  {red_light, green_light, yellow_light} = 3'b000;
  unique case (1'b1) // reversed case statement
    State[R_BIT]: red_light = 1'b1;
    State[G_BIT]: green_light = 1'b1;
    State[Y_BIT]: yellow_light = 1'b1;
  endcase
end: set_outputs
endmodule
```

Regular and Reversed Case Statements

```
module traffic_light (output logic green_light,
                      yellow_light,
                      red_light,
                      input sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input clock, resetN);

enum logic [2:0] {RED    = 3'b001, // explicit enum definition
                 GREEN  = 3'b010,
                 YELLOW = 3'b100} State, Next;

always_ff @(posedge clock, negedge resetN)
    if (!resetN) State <= RED; // reset to red light
    else          State <= Next;

always_comb begin: set_next_state
    Next = State; // the default for each branch below
    unique case (State)
        RED:    if (sensor)          Next = GREEN;
        GREEN:  if (green_downcnt == 0) Next = YELLOW;
        YELLOW: if (yellow_downcnt == 0) Next = RED;
    endcase
end: set_next_state

always_comb begin: set_outputs
    {green_light, yellow_light, red_light} = 3'b000;
    unique case (State)
        RED:    red_light  = 1'b1;
        GREEN:  green_light = 1'b1;
        YELLOW: yellow_light = 1'b1;
    endcase
end: set_outputs
endmodule
```

```
module traffic_light (output logic green_light,
                      yellow_light,
                      red_light,
                      input sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input clock, resetN);

enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;



// shift a 1 to the bit that represents each state
enum logic [2:0] {RED    = 3'b001<<R_BIT,
                 GREEN  = 3'b001<<G_BIT,
                 YELLOW = 3'b001<<Y_BIT} State, Next;

always_ff @(posedge clock, negedge resetN)
    if (!resetN) State <= RED; // reset to red light
    else          State <= Next;

always_comb begin: set_next_state
    Next = State; // the default for each branch below
    unique case (1'b1) // reversed case statement
        State[R_BIT]: if (sensor)          Next = GREEN;
        State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
        State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
    endcase
end: set_next_state

always_comb begin: set_outputs
    {red_light, green_light, yellow_light} = 3'b000;
    unique case (1'b1) // reversed case statement
        State[R_BIT]: red_light  = 1'b1;
        State[G_BIT]: green_light = 1'b1;
        State[Y_BIT]: yellow_light = 1'b1;
    endcase
end: set_outputs
endmodule
```


Regular and Reversed Case Statements

  

Reversed Case Statements

- A second enumerated type variable is declared that represents **the index number** for each bit of the one-hot State register.
- The name R_BIT has a value of 0, which corresponds to bit 0 of the State variable (the bit that represents the RED state).

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input      sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input      clock, resetN);

    enum {R_BIT = 0, // index of RED state in State register
          G_BIT = 1, // index of GREEN state in State register
          Y_BIT = 2} state_bit;

    // shift a 1 to the bit that represents each state
    enum logic [2:0] {RED    = 3'b001<<R_BIT,
                     GREEN  = 3'b001<<G_BIT,
                     YELLOW = 3'b001<<Y_BIT} State, Next;

    always_ff @(posedge clock, negedge resetN)
        if (!resetN) State <= RED; // reset to red light
        else          State <= Next;

    always_comb begin: set_next_state
        Next = State; // the default for each branch below
        unique case (1'b1) // reversed case statement
            State[R_BIT]: if (sensor)          Next = GREEN;
            State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
            State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
        endcase
    end: set_next_state

    always_comb begin: set_outputs
        {red_light, green_light, yellow_light} = 3'b000;
        unique case (1'b1) // reversed case statement
            State[R_BIT]: red_light  = 1'b1;
            State[G_BIT]: green_light = 1'b1;
            State[Y_BIT]: yellow_light = 1'b1;
        endcase
    end: set_outputs
endmodule
```

Reversed Case Statements with Enumerated Types

```
module traffic_light ( output logic green_light,
                      yellow_light,
                      red_light,
                      input sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input clock, resetN);

enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;

// shift a 1 to the bit that represents each state
enum logic [2:0] { RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

always_ff @(posedge clock, negedge resetN)
if (!resetN) State <= RED; // reset to red light
else State <= Next;

always_comb begin: set_next_state
Next = State; // the default for each branch below
```

- The enumerated variable `state_bit` specifies which bit of the state sequencer represents each state (the 1-hot bit).
- The value for each state label is calculated by shifting a 3-bit value of 001 (binary) to the bit position that is "hot" for that state.
- A value of 001 shifted 0 times (the value of `R_BIT`) is 001 (binary).
- A 001 shifted 1 time (the value of `G_BIT`) is 010 (binary), and shifted 2 times (the value of `Y_BIT`) is 100 (binary).
- The same enumerated `state_bit` labels, `R_BIT`, `G_BIT` and `Y_BIT`, are used in the functional code to test which bit of `State` is "hot".

Reversed Case Statements

- The enumerated variable `state_bit` specifies which bit of the state sequencer represents each state (the 1-hot bit).
- The value for each state label is calculated by **shifting** a 3-bit value of 001 (binary) to the bit position that is "hot" for that state.
 - A value of 001 shifted 0 times (the value of `R_BIT`) is 001 (binary).
 - A 001 shifted 1 time (the value of `G_BIT`) is 010 (binary), and
 - shifted 2 times (the value of `Y_BIT`) is 100 (binary).

```
module traffic_light (output logic green_light,
                     yellow_light,
                     red_light,
                     input
                     sensor,
                     input [15:0] green_downcnt,
                     yellow_downcnt,
                     input
                     clock, resetN);

enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;

// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

always_ff @(posedge clock, negedge resetN)
  if (!resetN) State <= RED; // reset to red light
  else
    State <= Next;

always_comb begin: set_next_state
  Next = State; // the default for each branch below
  unique case (1'b1) // reversed case statement
    State[R_BIT]: if (sensor) Next = GREEN;
    State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
    State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
  endcase
end: set_next_state

always_comb begin: set_outputs
  {red_light, green_light, yellow_light} = 3'b000;
  unique case (1'b1) // reversed case statement
    State[R_BIT]: red_light = 1'b1;
    State[G_BIT]: green_light = 1'b1;
    State[Y_BIT]: yellow_light = 1'b1;
  endcase
end: set_outputs
endmodule
```

Reversed Case Statements

- The same enumerated state_bit labels, R_BIT, G_BIT and Y_BIT, are used in the functional code to test which bit of State is "hot".
- The definitions of the enumerated labels for State and the bit-selects of the State variable are linked together by the definition of state_bit.
- Using this type of case statement ensures inference of efficient comparison logic that only does 1-bit comparisons against the onehot bits of the state and next vectors.

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input
                    sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input
                    clock, resetN);

enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;

// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

always_ff @(posedge clock, negedge resetN)
  if (!resetN) State <= RED; // reset to red light
  else
    State <= Next;

always_comb begin: set_next_state
  Next = State; // the default for each branch below
  unique case (1'b1) // reversed case statement
    State[R_BIT]: if (sensor) Next = GREEN;
    State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
    State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
  endcase
end: set_next_state

always_comb begin: set_outputs
  {red_light, green_light, yellow_light} = 3'b000;
  unique case (1'b1) // reversed case statement
    State[R_BIT]: red_light = 1'b1;
    State[G_BIT]: green_light = 1'b1;
    State[Y_BIT]: yellow_light = 1'b1;
  endcase
end: set_outputs
endmodule
```

Reverse Case Statement

```
enum {  
  IDLE = 0,  
  READ = 1,  
  DLY = 2,  
  DONE = 3  
} state, next;  
  
// Sequential state transition  
always_ff @(posedge clk or negedge rst_n)  
  if (!rst_n) begin  
    state <= '0; // default assignment  
    state[IDLE] <= 1'b1;  
  end  
  else  
    state <= next;
```

- The state enumerated type values represent *indices* into the *state* and *next* vectors.
- Synthesis tools efficiently generate output assignment and next state logic that *does only 1-bit comparison against the state vectors*.

```
// Combinational next state logic  
always_comb begin  
  next = '0;  
  unique case (1'b1)  
    state[IDLE] : begin  
      if (go)  
        next[READ] = 1'b1;  
      else  
        next[IDLE] = 1'b1;  
      end  
    state[READ] : next[DLY] = 1'b1;  
    state[DLY] : begin  
      if (!ws)  
        next[DONE] = 1'b1;  
      else  
        next[READ] = 1'b1;  
      end  
    state[DONE] : next[IDLE] = 1'b1;  
  endcase  
end  
  
// Make output assignments  
always_ff @(posedge clk or negedge rst_n)  
  ...
```

Reversed Case Statements with Enumerated Types

```
enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;
// shift a 1 to the bit that represents each state
enum logic [2:0] { RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

.....
always_comb begin: set_next_state
Next = State; // the default for each branch below
unique case (1'b1) // reversed case statement
State[R_BIT]: if (sensor) Next = GREEN;
State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
endcase
end: set_next_state

.....
```

- This scheme serves two important purposes:
 - There is no possibility of a coding error that defines different 1-hot bit positions in the two enumerated type definitions.
 - Should the design specification change the 1-hot definitions, only the enumerated type specifying the bit positions has to change.
- The enumerated type defining the state names will automatically reflect the change.

Reversed Case Statements with Verilog

```
module fsm_cc1_3oh
(output reg rd, ds,
 input   go, ws, clk, rst_n);
parameter IDLE = 0,
           READ = 1,
           DLY  = 2,
           DONE = 3;
reg [3:0] state, next;
always @(posedge clk or negedge rst_n)
  if (!rst_n) begin
    state    <= 4'b0;
    state[IDLE] <= 1'b1;
  end
  else      state    <= next;
always @(state or go or ws) begin
  next = 4'b0;
  case (1'b1) // synopsys parallel_case
    state[IDLE] : if (go) next[READ] = 1'b1;
                  else  next[IDLE] = 1'b1;
    state[READ] :      next[ DLY] = 1'b1;
```

```
    state[ DLY] : if (!ws) next[DONE] = 1'b1;
                  else  next[READ] = 1'b1;
    state[DONE] :      next[IDLE] = 1'b1;
  endcase
end
always @(posedge clk or negedge rst_n)
  if (!rst_n) begin
    rd <= 1'b0;
    ds <= 1'b0;
  end
  else begin
    rd <= 1'b0;
    ds <= 1'b0;
    case (1'b1) // synopsys parallel_case
      next[READ] : rd <= 1'b1;
      next[ DLY] : rd <= 1'b1;
      next[DONE] : ds <= 1'b1;
    endcase
  end
endmodule
```




Miscellaneous on Modeling FSMs in SV



Unused States

- As an enumerated type, the State variable has a restricted set of values.
- The State variable is a multi-bit vector, which, at the gate-level, can reflect logic values not defined in the enumerated list.
- A FSM with three states requires a 3-bit state register for one-hot encoding.
 - This 3-bit register can contain 8 possible values.
- The hardware registers represented can hold all possible values, not just the values listed in the enumerated list.

Unused States: Enumerated Types with logic

```
// case statement with enumerated X default
enum logic [2:0] { RED = 3'b001,
                  GREEN = 3'b010,
                  YELLOW = 3'b100,
                  BAD_STATE = 3'bxxx,
                  } State, Next;

case (State)
  RED: Next = GREEN;
  GREEN: Next = YELLOW;
  YELLOW: Next = RED;
  default: Next = BAD_STATE;
endcase
```

- In SV, an enumerated type can **only be assigned values from its enumerated list**.
- If an X assignment is desired, the base type of the enumerated type must be defined a 4-state type, such as **logic**, and an enumerated label must be defined with an **explicit value of X**.

Unused States: A Better SV Solution

// case statement with enumerated X default

```
enum logic [2:0] { RED = 3'b001,  
                  GREEN = 3'b010,  
                  YELLOW = 3'b100,  
                  BAD_STATE = 3'bxxx,  
                  } State, Next;
```



```
case (State)  
  RED: Next = GREEN;  
  GREEN: Next = YELLOW;  
  YELLOW: Next = RED;  
  default: Next = BAD_STATE;  
endcase
```



// unique case statement

```
enum logic [2:0] { RED = 3'b001,  
                  GREEN = 3'b010,  
                  YELLOW = 3'b100,  
                  } State, Next;
```

```
unique case (State)  
  RED: Next = GREEN;  
  GREEN: Next = YELLOW;  
  YELLOW: Next = RED;  
endcase
```

Assigning State Values to Enumerated Variables

- Assignments with Enumerated Type Variables:
 - Enumerated types are more **strongly typed** than other Verilog and SystemVerilog variables.
 - Enumerated types can only be assigned a value that is a member of the type list of that enumerated type.
 - An enumerated type can be assigned the value of another enumerated type, but only if both enumerated types are from the same definition.

Enumerated Assignments: Illegal

```
enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;
// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

...
always_comb begin: set_next_state
  Next = 3'b000; // clear Next - ERROR: ILLEGAL ASSIGNMENT
  unique case (1'b1) // reversed case statement
  // WARNING: FOLLOWING ASSIGNMENTS ARE POTENTIAL DESIGN ERRORS
  State[R_BIT]: if (sensor == 1) Next[G_BIT] = 1'b1;
  State[G_BIT]: if (green_downcnt==0) Next[Y_BIT] = 1'b1;
  State[Y_BIT]: if (yellow_downcnt==0) Next[R_BIT] = 1'b1;
  endcase
end: set_next_state

...
```

- A common Verilog style when using one-hot state sequences is to first **clear the next state variable**, and then set just the one bit of next state variable that indicates what the next state will be.
- This style will not work with enumerated types.
- Two problems:
 - First, a default assignment of all zeros is made to the Next variable.
 - This is **an illegal assignment**.
 - An enumerated type must be assigned labels **from its enumerated list, not literal values**.

Enumerated Assignments: Legal but not Recommended

```
enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;
// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

...
always_comb begin: set_next_state
  Next = 3'b000; // clear Next - ERROR: ILLEGAL ASSIGNMENT
  unique case (1'b1) // reversed case statement
  // WARNING: FOLLOWING ASSIGNMENTS ARE POTENTIAL DESIGN ERRORS
  State[R_BIT]: if (sensor == 1) Next[G_BIT] = 1'b1;
  State[G_BIT]: if (green_downcnt==0) Next[Y_BIT] = 1'b1;
  State[Y_BIT]: if (yellow_downcnt==0) Next[R_BIT] = 1'b1;
  endcase
end: set_next_state

...
```

- Second, within the case statements, assignments are made to individual bits of the Next variable.
- Assigning to a discrete bit of an enumerated type **MAY be allowed by compilers**, but it is not a good style when using enumerated types.
- By assigning to a bit of an enumerated type variable, an illegal value could be created that is not in the enumerated type list.
- This would result in design errors that could be difficult to debug.

The Correct One: Use its Labels

- Assignments to enumerated type variables should be from **the list of labels for that type**.
- Assigning to bit-selects or part-selects of an enumerated type should be avoided.
- When assignments to bits of a variable are required, the variable should be declared as standard type, such as bit or logic, instead of an enumerated type.
- *Assign an enumerated type variable a label from its enumerated list, instead of a value.*

```
module traffic_light (output logic green_light,
                    yellow_light,
                    red_light,
                    input      sensor,
                    input [15:0] green_downcnt,
                    yellow_downcnt,
                    input      clock, resetN);

    enum {R_BIT = 0, // index of RED state in State register
          G_BIT = 1, // index of GREEN state in State register
          Y_BIT = 2} state_bit;

    // shift a 1 to the bit that represents each state
    enum logic [2:0] {RED   = 3'b001<<R_BIT,
                     GREEN  = 3'b001<<G_BIT,
                     YELLOW = 3'b001<<Y_BIT} State, Next;

    always_ff @(posedge clock, negedge resetN)
        if (!resetN) State <= RED; // reset to red light
        else          State <= Next;

    always_comb begin: set_next_state
        Next = State; // the default for each branch below
        unique case (1'b1) // reversed case statement
            State[R_BIT]: if (sensor)           Next = GREEN;
            State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
            State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
        endcase
    end: set_next_state

    always_comb begin: set_outputs
        {red_light, green_light, yellow_light} = 3'b000;
        unique case (1'b1) // reversed case statement
            State[R_BIT]: red_light  = 1'b1;
            State[G_BIT]: green_light = 1'b1;
            State[Y_BIT]: yellow_light = 1'b1;
        endcase
    end: set_outputs
endmodule
```


The Correct One: Use its Labels

```
enum {R_BIT = 0, // index of RED state in State register
      G_BIT = 1, // index of GREEN state in State register
      Y_BIT = 2} state_bit;

// shift a 1 to the bit that represents each state
enum logic [2:0] {RED = 3'b001<<R_BIT,
                  GREEN = 3'b001<<G_BIT,
                  YELLOW = 3'b001<<Y_BIT} State, Next;

...

always_comb begin: set_next_state
    Next = 3'b000; // clear Next - ERROR: ILLEGAL
    ASSIGNMENT
    unique case (1'b1) // reversed case statement
    // WARNING: FOLLOWING ASSIGNMENTS ARE
    // POTENTIAL DESIGN ERRORS
    State[R_BIT]: if (sensor == 1) Next[G_BIT] = 1'b1;
    State[G_BIT]: if (green_downcnt==0) Next[Y_BIT] = 1'b1;
    State[Y_BIT]: if (yellow_downcnt==0) Next[R_BIT] = 1'b1;
    endcase
end: set_next_state

...
```

```
module traffic_light (output logic green_light,
                      yellow_light,
                      red_light,
                      input sensor,
                      input [15:0] green_downcnt,
                      yellow_downcnt,
                      input clock, resetN);

    enum {R_BIT = 0, // index of RED state in State register
          G_BIT = 1, // index of GREEN state in State register
          Y_BIT = 2} state_bit;

    // shift a 1 to the bit that represents each state
    enum logic [2:0] {RED = 3'b001<<R_BIT,
                      GREEN = 3'b001<<G_BIT,
                      YELLOW = 3'b001<<Y_BIT} State, Next;

    always_ff @(posedge clock, negedge resetN)
        if (!resetN) State <= RED; // reset to red light
        else State <= Next;

    always_comb begin: set_next_state
        Next = State; // the default for each branch below
        unique case (1'b1) // reversed case statement
            State[R_BIT]: if (sensor) Next = GREEN;
            State[G_BIT]: if (green_downcnt == 0) Next = YELLOW;
            State[Y_BIT]: if (yellow_downcnt == 0) Next = RED;
        endcase
    end: set_next_state

    always_comb begin: set_outputs
        {red_light, green_light, yellow_light} = 3'b000;
        unique case (1'b1) // reversed case statement
            State[R_BIT]: red_light = 1'b1;
            State[G_BIT]: green_light = 1'b1;
            State[Y_BIT]: yellow_light = 1'b1;
        endcase
    end: set_outputs
endmodule
```

Lock-up with Default Values

```
enum {WAITE, LOAD, STORE} State, Next;
always @(posedge clock, negedge resetN)
if (!resetN) State <= WAITE;
    else State <= Next;
always @(State)
    case (State)
        WAITE: Next = LOAD;
        LOAD: Next = STORE;
        STORE: Next = WAITE;
    endcase
```

- Both State and Next variables begin simulation with a value of 0,
 - = WAITE = 0 .
- At every positive edge of clock,
 - State <= Next (0)
 - the value it already has
 - no transition occurs.
- Since there is no transition,
 - always @(State) is not triggered
 - Next is not changed from its initial value of 0.

Solution: logic type

```
enum {WAITE, LOAD, STORE} State, Next;  
always @(posedge clock, negedge resetN)  
if (!resetN) State <= WAITE;  
    else State <= Next;  
always @(State)  
    case (State)  
        WAITE: Next = LOAD;  
        LOAD: Next = STORE;  
        STORE: Next = WAITE;  
    endcase
```



```
enum logic[1:0] {WAITE, LOAD, STORE} State,  
Next;  
always @(posedge clock, negedge resetN)  
if (!resetN) State <= WAITE;  
    else State <= Next;  
always @(State)  
    case (State)  
        WAITE: Next = LOAD;  
        LOAD: Next = STORE;  
        STORE: Next = WAITE;  
    endcase
```

- Simulation will then begin with State and Next having an un-initialized value of X.
- In RTL simulation, when reset is applied, the State variable will transition from X to its reset value of WAITE (=00).
 - This transition will trigger the logic that decodes Next, setting Next to its appropriate value of LOAD.

Solution: always_comb

```
enum {WAITE, LOAD, STORE} State, Next;  
always @(posedge clock, negedge resetN)  
if (!resetN) State <= WAITE;  
    else State <= Next;  
always @(State)  
    case (State)  
        WAITE: Next = LOAD;  
        LOAD: Next = STORE;  
        STORE: Next = WAITE;  
    endcase
```



```
enum {WAITE, LOAD, STORE} State, Next;  
always @(posedge clock, negedge resetN)  
if (!resetN) State <= WAITE;  
    else State <= Next;  
always_comb  
    case (State)  
        WAITE: Next = LOAD;  
        LOAD: Next = STORE;  
        STORE: Next = WAITE;  
    endcase
```

- An `always_comb` block automatically executes its statements once at simulation time zero, even if there were no transitions on its inferred sensitivity list.
 - The initial value of `State` will be decoded, and the `Next` variable set accordingly.
- This fixes the start of simulation lock-up problem.

A SV Robust Solution

```
enum logic[1:0] {WAITE, LOAD, STORE}
State, Next;
always @(posedge clock, negedge resetN)
if (!resetN) State <= WAITE;
    else State <= Next;
always_comb
    case (State)
        WAITE: Next = LOAD;
        LOAD: Next = STORE;
        STORE: Next = WAITE;
    endcase
```



```
enum logic[1:0] {WAITE, LOAD, STORE} State, Next;
always_ff @(posedge clock, negedge resetN)
if (!resetN) State <= WAITE;
    else State <= Next;
always_comb
    unique case (State)
        WAITE: Next = LOAD;
        LOAD: Next = STORE;
        STORE: Next = WAITE;
    endcase
```

- If State had not been reset, it would be a logic X, which will not match any of the case items to which State is compared.
- The unique case (State) statement will issue a run-time warning whenever no case items match the case expression.
- A warning would also be issued if the case expression matches more than one case item.

A SV Robust Solution

```
enum logic[1:0] {WAITE, LOAD, STORE} State, Next;
always_ff @(posedge clock, negedge resetN)
if (!resetN) State <= WAITE;
    else State <= Next;
always_comb
    unique case (State)
        WAITE: Next = LOAD;
        LOAD: Next = STORE;
        STORE: Next = WAITE;
    endcase
```

- A SV Robust Solution:
 - Combining Unique Case with a logic based Enumerated Types
- This combination of SV constructs not only simplifies writing RTL code, it can trap design problems that could have been difficult to detect and debug in Verilog.

References

- SystemVerilog for Design, by Stuart Sutherland et al.
- "Synthesizable Finite State Machine Design Techniques" by Clifford E. Cummings, Sunburst Design, Inc. 2003.
- "Synthesizing SystemVerilog" by S. Sutherland, D. Mills. 2013.
- Sutherland, "SystemVerilog Saves the Day—the Evil Twins are Defeated! unique and priority" are the new Heroes", Synopsys Users Group (SNUG) conference, San Jose, California, March 2005.
- Mills and Sutherland, "SystemVerilog Assertions Are For Design Engineers Too!", Synopsys Users Group (SNUG) conference, San Jose, California, March 2006.
- Mills, "Being assertive with your X (SystemVerilog assertions for dummies)", Synopsys Users Group Conference (SNUG) San Jose, California, 2004.
- Mills, "Yet Another Latch and Gotchas Paper", Synopsys Users Group (SNUG) conference, San Jose, California, March 2012.
- Sutherland, "I'm Still in Love with My X!", Design and Verification Conference (DVCon), San Jose, California, February 2013.
- Greene, Salz and Booth, "X-Optimism Elimination during RTL Verification", Synopsys Users Group Conference (SNUG) San Jose, 2012.